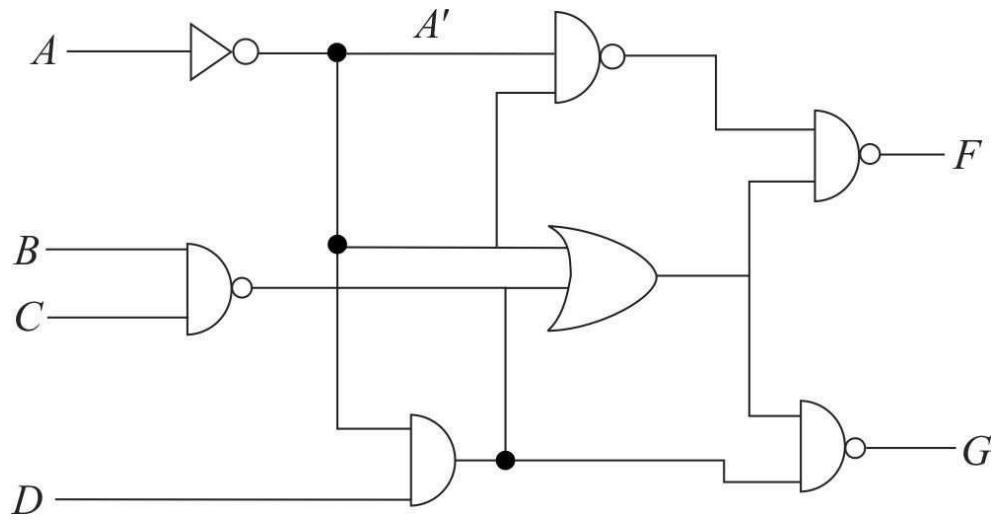


4.2



$$F(A, B, C, D) = ((A'D)' (A' + BC))'$$

$$= A'D + (A' + BC)'$$

$$= A'D + A(BC)'$$

$$= A'D + AB' + AC'$$

$$C1(A, B, C, D) = ((A'D) (A' + BC))'$$

$$= (A'D)' + (A' + BC)'$$

$$= (A + D') + A(BC)'$$

$$= A + D' + AB' + AC'$$

$$= A(1 + B' + C') + D'$$

$$= A + D'$$

4.4


(a) $F(A, B, C) = \Sigma(0, 1, 2, 7)$

	BC			
A	00	01	01	10
$A'C'$	1	1	0	1
$A'B'$	0	0	1	0
			ABC	

Simplified SOP form:


$$\begin{aligned}
 F(A, B, C) &= A'C' + A'B' + ABC \\
 &= A'(B' + C') + ABC \\
 &= A'(BC)' + ABC \\
 &= \underline{A \text{ XNOR } (BC)}
 \end{aligned}$$

$$= A \oplus (BC)$$

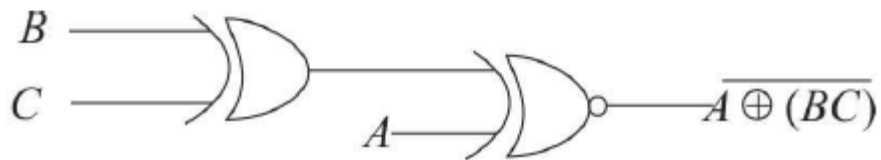


4.9


<i>ABCD</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	1	0	1	1

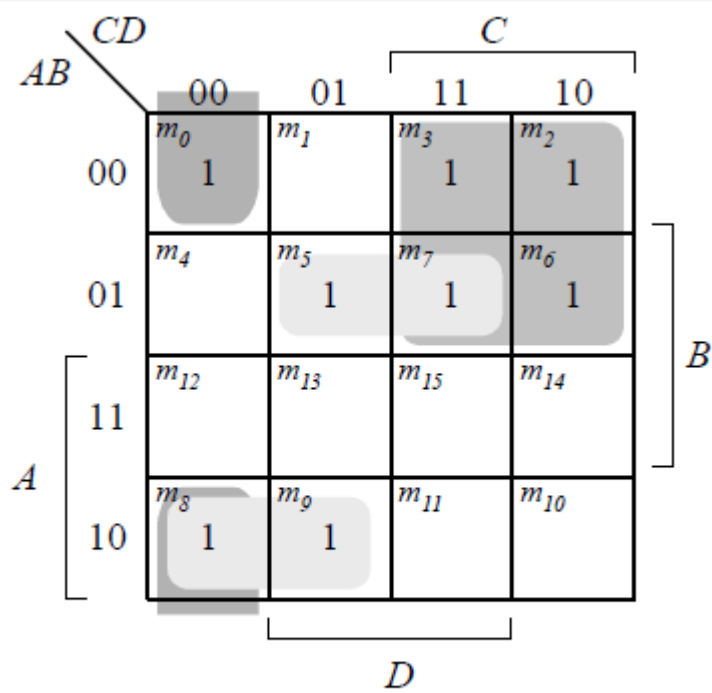


$$a = A'C + A'BD + B'C'D' + AB'C'$$

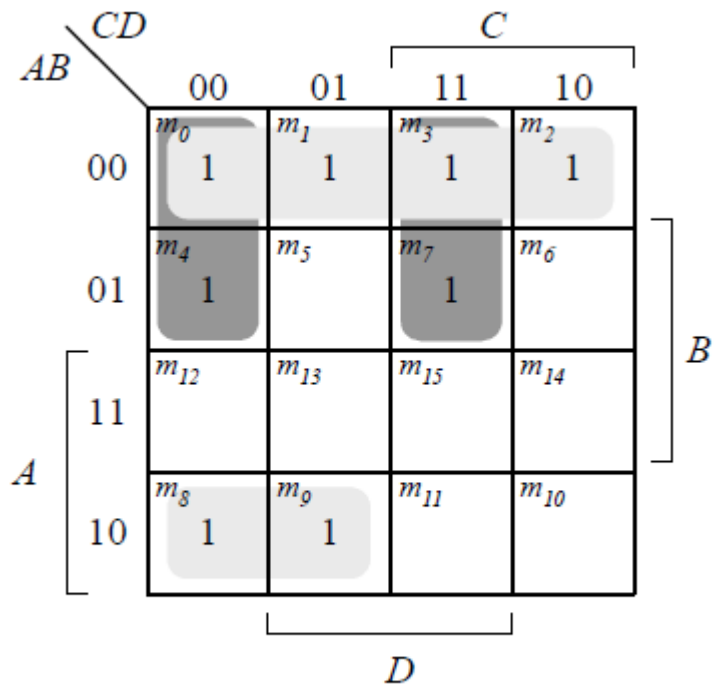


$$b = A'B' + A'C'D' + A'CD + AB'C'$$

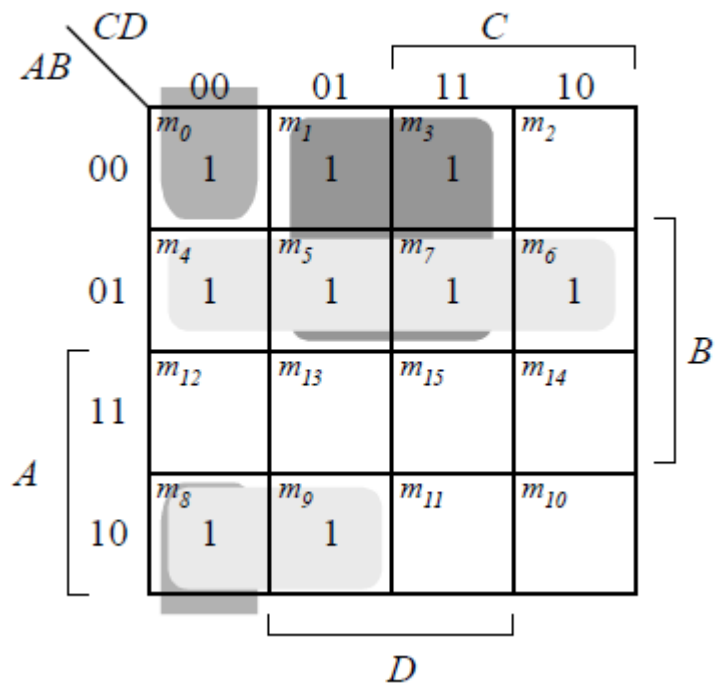


$$c = A'B + A'D + B'C'D' + AB'C'$$

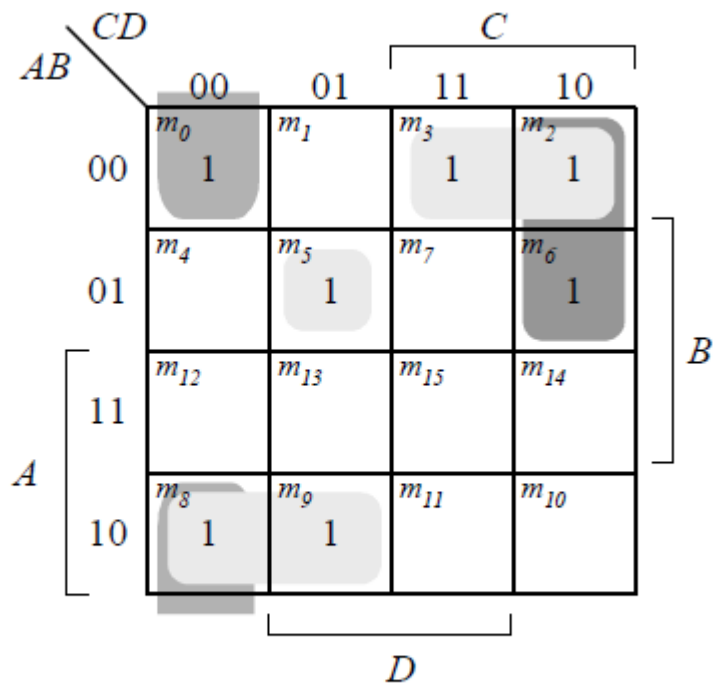

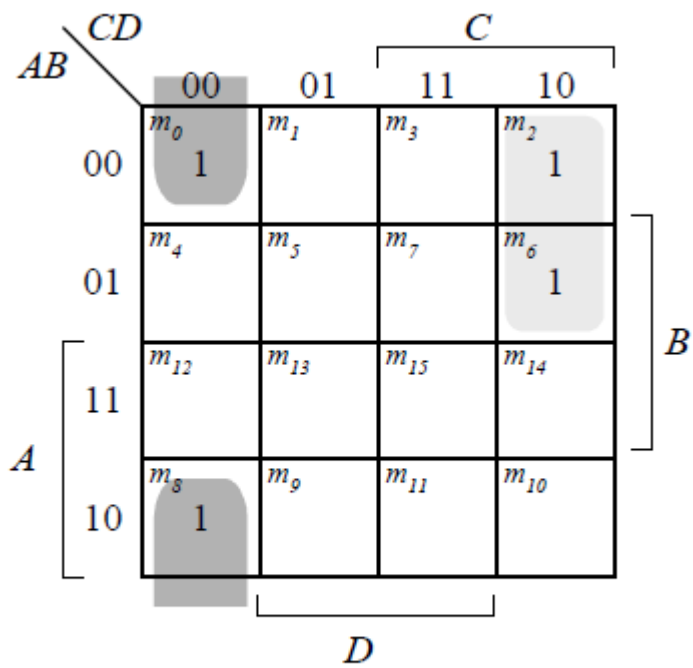
$$d = A'CD' + A'B'C + B'C'D' + AB'C' + A'BC'D$$



$$e = A'CD' + B'C'D'$$

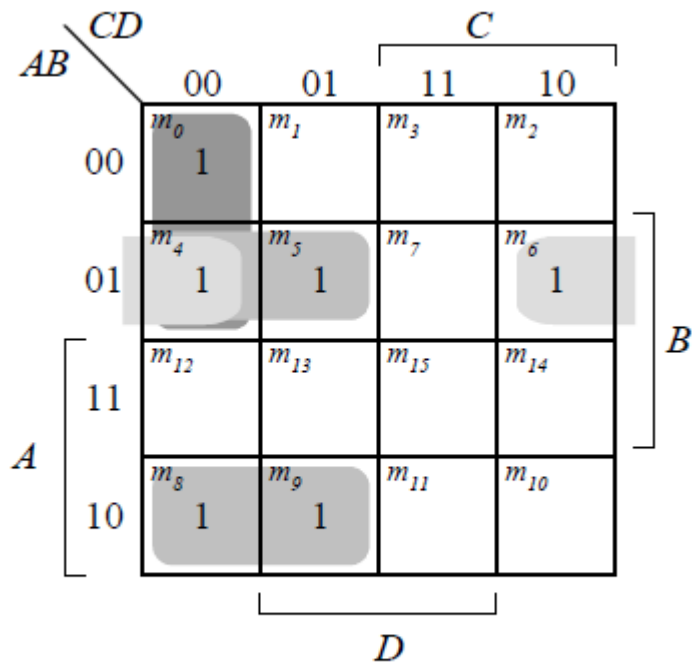

$$f = A'BC' + A'C'D' + A'BD + AB'C'$$

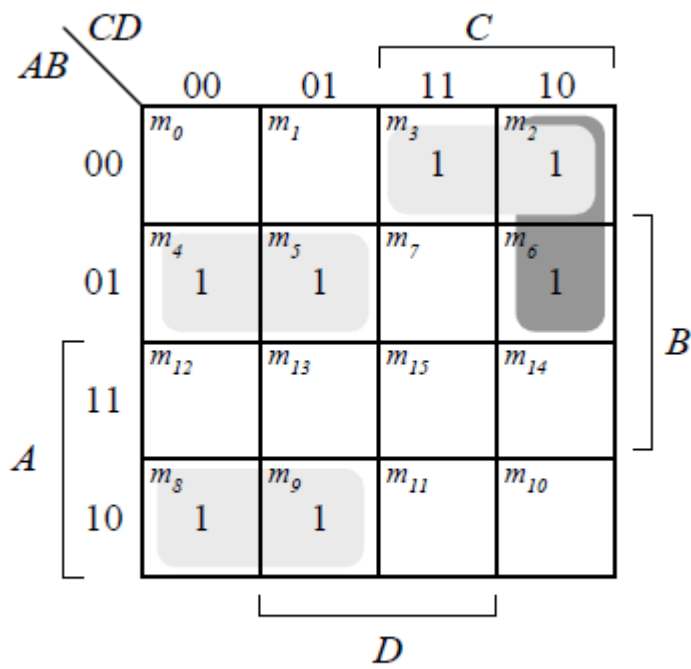

$$g = A'CD' + A'B'C + A'BC' + AB'C'$$

4.16

(a)

$$(C'G'i + p'i)' = (C_i + G_i)P_i = G_iP_i + P_iC_i$$

$$= A_iB_i(A_i + B_i) + P_iC_i$$

$$= A_iB_i + P_iC_i = G_i + P_iC_i$$

$$= A_iB_i + (A_i + B_i)C_i = A_iB_i + A_iC_i + B_iC_i = C_{i+1}$$

$$(P_iG'i) \oplus C_i = (A_i + B_i)(A_iB_i)' \oplus C_i = (A_i + B_i)(A_i' + B_i') \oplus C_i$$

$$= (A_i'B_i + A_iB_i') \oplus C_i = A_i \oplus B_i \oplus C_i = S_i$$

(b)

Output of NOR gate = $(A_0 + B_0)' = P_0$

Output of NAND gate = $(A_0B_0)' = G_0$

$S_1 = (P_0G_0) \oplus C_0$

$C_1 = (C_0G_0 + P_0)'$ as defined in part (a)

4.32

(a) $F = S(0, 2, 5, 8, 10, 14)$

Inputs ABCD	Mux input line (ABC) Value	$F = \Sigma(0, 2, 5, 8, 10, 14)$
000 0	0	1 $F = D'$
000 1	1	0
001 0	2	1 $F = D'$
001 1	3	0
010 0	4	0 $F = D$
010 1	5	1
011 0	6	0 $F = 0$
011 1	7	0
100 0	8	1 $F = D'$
100 1	9	0
101 0	10	1 $F = D'$
101 1	11	0
110 0	12	0 $F = 0$
110 1	13	0
111 0	14	1 $F = D'$
111 1	15	0

